 


## 6. Sequential Circuit

- Q.1** Refer to the NAND and NOR latches shown in the figure. The input  $(P_1, P_2)$  for both the latches are first made  $(0, 1)$  and then, after a few seconds, made  $(1, 1)$ . The corresponding stable output  $(Q_1, Q_2)$  are

[GATE 2009, IIT Roorkee]



- (A) NAND: first  $(0, 1)$  then  $(0, 1)$  NOR : first  $(1, 0)$  then  $(0, 0)$ .  
 (B) NAND: first  $(1, 0)$  then  $(1, 0)$  NOR : first  $(1, 0)$  then  $(1, 0)$ .  
 (C) NAND: first  $(1, 0)$  then  $(1, 0)$  NOR : first  $(1, 0)$  then  $(0, 0)$ .  
 (D) NAND: first  $(1, 0)$  then  $(1, 1)$  NOR : first  $(0, 1)$  then  $(0, 1)$ .

- Q.2** Two  $D$  flip-flops are connected as a synchronous counter that goes through the following  $Q_B Q_A$  sequence  
 $00 \rightarrow 11 \rightarrow 01 \rightarrow 10 \rightarrow 00 \rightarrow \dots$

The connections to the inputs  $D_A$  and  $D_B$  are

[GATE 2011, IIT Madras]

- (A)  $D_A = Q_B, D_B = Q_A$  (B)  $D_A = \overline{Q_A}, D_B = \overline{Q_B}$   
 (C)  $D_A = (Q_A \overline{Q_B} + \overline{Q_A} Q_B), D_B = Q_A$  (D)  $D_A = (Q_A Q_B + \overline{Q_A} \overline{Q_B}), D_B = \overline{Q_B}$

**Q.3** The next state table of a 2-bit saturating up- counter is given below.


$Q_1$	$Q_0$	$Q_1^+$	$Q_0^+$
0	0	0	1
0	1	1	0
1	0	1	1
1	1	1	1

The counter is built as a synchronous sequential circuit using  $T$  flip-flops. The expression for  $T_1$  and  $T_0$  are

[GATE 2017, IIT Roorkee]

- (A)  $T_1 = Q_1 Q_0, T_0 = \overline{Q_1} \overline{Q_0}$  (B)  $T_1 = \overline{Q_1} Q_0, T_0 = \overline{Q_1} + \overline{Q_0}$   
 (C)  $T_1 = Q_1 + Q_0, T_0 = \overline{Q_1} + \overline{Q_0}$  (D)  $T_1 = \overline{Q_1} Q_0, T_0 = Q_1 + Q_0$

**Q.4** Consider the following circuit.

 


The flip-flops are positive edge triggered D FFs. Each state is designated as a two bit string  $Q_0 Q_1$ . Let the initial state be 00. The state transition sequence is

[GATE 2005, IIT Bombay]

- (A)  $00 \rightarrow 11 \rightarrow 01$  (B)  $00 \rightarrow 11$  (C)  $00 \rightarrow 10 \rightarrow 01 \rightarrow 11$  (D)  $00 \rightarrow 11 \rightarrow 01 \rightarrow 10$

 **Q.5** A 2-bit counter circuit is shown below,








If the state  $Q_A Q_B$  of the counter at the clock time  $t_n$  is "10" then the state  $Q_A Q_B$  of the counter at  $t_n + 3$  (after three cycles) will be

[GATE 2011, IIT Madras]


- (A) 00 (B) 01 (C) 10 (D) 11

 **Q.6** The state transition diagram for the logic circuit shown is [GATE 2012, IIT Delhi]



    

 **Q.7** A finite state machine (FSM) is implemented using the  $D$  flip-flops  $A$  and  $B$  and logic gates, as shown in the figure below. The four possible states of the FSM are  $Q_A Q_B = 00, 01, 10$  and  $11$ .




Assume that  $X_{IN}$  is held at a constant logic level throughout the operation of the FSM. When the FSM is initialized to the state  $Q_A Q_B = 00$  and clocked, after a few clock cycles, it starts cycling through

[GATE 2017, IIT Roorkee]

- (A) all of the four possible states if  $X_{IN} = 1$ . (B) three of the four possible states if  $X_{IN} = 0$ .  
 (C) only two of the four possible states if  $X_{IN} = 1$ . (D) only two of the four possible states if  $X_{IN} = 0$ .


**Q.8** The ripple counter shown in figure is made up of negative edge triggered  $J-K$  flip-flops. The signals levels at  $J$  and  $K$  inputs of all the flip-flops are maintained at logic 1. Assume all the outputs are cleared just prior to applying the clock signal. Module number of the counter is

[GATE 2002, IISc Bangalore]

 

- (A) 7 (B) 5 (C) 4 (D) 8

 **Q.9** The ripple counter shown in the given figure is works as a [GATE 1999, IIT Bombay]




- (A) MOD-3 up counter.  
(C) MOD-3 down counter.

 - (B) MOD-5 up counter.  
(D) MOD-5 down counter.

**Common Data for  
Questions 10 & 11**

Consider the counter circuit shown below.



**Q.10** In the above figure, Y can be expressed as

[GATE 2008, IISc Bangalore]


- (A)  $Q_3 \cdot (Q_1 + Q_2)$  (B)  $Q_3 + Q_1 \cdot Q_2$  (C)  $\overline{Q_3} \cdot (Q_1 + Q_2)$  (D)  $\overline{Q_3} + Q_1 \cdot Q_2$

**Q.11** The above circuit is a

[GATE 2008, IISc Bangalore]

- (A) Mod-8 Counter (B) Mod-9 Counter (C) Mod-10 Counter (D) Mod-11 Counter

**Q.12** In the modulo-6 ripple counter shown in below, figure the output of the 2-input gate is used to clear the J-K flip-flops.

 


The 2-input gate is

[GATE 2004, IIT Delhi]

- (A) a NAND gate (B) a NOR gate (C) an OR gate (D) an AND gate

**Q.13** In the figure, the J and K inputs of all the four flip-flops are made high. The frequency of the signal at output Y is


[GATE 2000, IIT Kharagpur]

 

- (A) 0.833 kHz (B) 1.0 kHz (C) 0.91 kHz (D) 0.77 kHz

**Q.14** Which one of the following statements is true about the digital circuit shown in the figure.


[GATE 2018, IIT Guwahati]

 

- (A) It can be used for dividing the input frequency by 3.
- (B) It can be used for dividing the input frequency by 5.
- (C) It can be used for dividing the input frequency by 7.
- (D) It cannot be reliably used as a frequency divider due to disjoint internal cycles.

**Q.15** The initial contents of the 4-bit serial-in-parallel-out, right-shift, Shift Register shown in the figure is 0110. After three clock pulses are applied, the contents of the Shift Register will be


[GATE 1992, IIT Delhi]

 

- (A) 0000
- (B) 0101
- (C) 1010
- (D) 1111



# Sequential Circuit

 

② NAND - (1,0) then (1,0)  
 NOR - (1,0) then (0,0)

OK

③

00 → 11 → 01 → 10 → 00 → ...

$D_A, D_B = ?$

Sol<sup>n</sup>

$Q_0$	$Q_1$	$Q_{n+1}$	$Q_{n+1}$	$D_B$	$D_A$
0	0	1	1	1	1
0	1	1	0	1	0
1	0	0	0	0	0
1	1	0	1	0	1

$D_A = (Q_1 Q_0 + \bar{Q}_1 \bar{Q}_0), D_B = \bar{Q}_0$

3)


8)

$Q_1$	$Q_0$	$Q_1^+$	$Q_0^+$	$T_1$	$T_0$
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	0	0

$T_1 = \overline{Q_1} Q_0, T_0 = \overline{Q_1} + \overline{Q_0}$  Ans


4)

9)

 

$Q_0$	$Q_1$	$Q_0^+$	$Q_1^+$
0	0	1	1
0	1	1	0
1	0	0	0
1	1	0	1

 
$Q_0^+ = D_0 = \overline{Q_0}$   
 $Q_1^+ = D_1$   
 $= Q_0 \oplus Q_1$   
 $= Q_0 \odot Q_1$



Ans




5

 


$$Q_{A+1} = \overline{0A} + 1A \cdot Q_A$$

$$= \overline{0B} \cdot \overline{0A} + \overline{0B} \cdot 0A$$

$$= \overline{0B}$$

 


$$Q_{B+1} = Q_B \oplus Q_A$$

 

$$Q_{3+n} = 10$$

6

 


$$Q_{n+1} = D = Y = X_0$$

$$Q_{n+1} = Q_n \quad A=1$$

$$Q_{n+1} = D = Y = X_0 = \overline{Q_n} \quad A=0$$

$$Q_{n+1} = \overline{Q_n}$$

 



7

8

$Q_A$	$Q_B$	$Q_{A+1}$	$Q_{B+1}$
0	0	0	1
0	1	1	1
1	0	1	1
1	1	0	1

$$Q_{A+1} = P_A = Q_A \oplus Q_B$$



$$X_{in} = 0$$

$$Q_{B+1} = D_B = 1$$

$$Q_{A+1} = P_A = Q_A \oplus Q_B$$

$$X_{in} = 1$$

$$Q_{B+1} = D_B = \overline{Q_A}$$

  

2nd step

Only 2 ~~steps~~ possible st  
if  $X_{in} = 0$

Ans

Q3

B

$Q_2$	$Q_1$	$Q_0$	$\overline{Q_2}$	$\overline{Q_0}$
0	0	0	1	
0	0	1	1	
0	1	0	1	
0	1	1	1	
1	0	0	1	
1	0	1	0	
1	1	0		
1	1	1		

5

up-counter

Q3

B

$Q_C$	$Q_B$	$Q_A$	$\overline{Q_C}$	$\overline{Q_B}$	$\overline{Q_A}$
1	1	1	0		
1	1	0	0		
1	0	1	0		
1	0	0	0		
0	1	1	0		
0	1	0	1		

5

Mod-5 down-counter



$Q_3$	$Q_2$	$Q_1$	$Q_0$	$S_3 (Q_2 + Q_1)$
0	0	0	0	1
0	0	0	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0

10

up-counter

Note:

If  $Q_1 = 1$  then synchronous clear / synchronous preset

then counter + 1

10 + 1 = 11

But not synchronous

so - mod-10 counter




12

$\overline{C} \rightarrow$  NAND

$$\overline{C} \cdot B \rightarrow \overline{C+B} = \overline{C} + \overline{B}$$

$\overline{C} \cdot B$  present

 

NOR GATE

13

$$f_{msb} = \frac{f_{clock}}{\text{mod } N_U}$$

$$f_{Q3} = f_y = \frac{10 \text{ KHz}}{10}$$

$$f_y = 1 \text{ KHz}$$


14

$$Q_{A+1} = D_A = \overline{Q_B \cdot Q_C}$$

$$Q_{B+1} = D_B = Q_A$$

$$Q_{C+1} = D_C = Q_B$$

$Q_1$	$Q_0$	$Q_c$	$Q_{A+1}$	$Q_{B+1}$	$Q_{C+1}$
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	1	1

 


$$F_{msb} = \frac{F_{clock}}{\text{Mod No}} = \frac{F_{clock}}{5}$$

It can be used dividing i/p frequency by 5

Ans



 

c ⊕ d

	A	B	C	D
	0	1	1	0
$1 \oplus 0 \longrightarrow$	1	0	1	1
$1 \oplus 1 \longrightarrow$	0	1	0	1
$0 \oplus 1 \longrightarrow$	1	0	1	0

→ Ans → 1010 Ans