 


## Chapter - 5 : Sequential Circuit

Q.98 For the initial state of 000, the function performed by the arrangement of the J-K flip-flops in figure is:

[GATE : 1993]



1	1	0	0
2	1	1	0
3	1	1	1
4	0	1	1
5	0	0	1
6	0	0	0

- (A) Shift Register (B) Mod-3 Counter (C) Mod-6 Counter (D) Mod-2 Counter

Q.99 Consider a 4-bit Johnson counter with an initial value of 0000. The counting sequence of this counter is

[GATE : 2015]

- (A) 0, 1, 3, 7, 15, 14, 12, 8, 0 (B) 0, 1, 3, 5, 7, 9, 11, 13, 15, 0  
(C) 0, 2, 4, 6, 8, 10, 12, 14, 0 (D) 0, 8, 12, 14, 15, 7, 3, 1, 0

Q.100 The minimum number of J-K flip-flops required to construct a synchronous counter with the count sequence (0, 0, 1, 1, 2, 2, 3, 3, 0, 0, ...) is 3.


[GATE : 2015]

Q.101 We want to design a synchronous counter that counts the sequence 0-1-0-2-0-3 and then repeats. The minimum number of J-K flip-flops required to implement this counter is 4.

[GATE : 2016]

Q.102 Consider the circuit given below with initial state  $Q_0 = 1, Q_1 = Q_2 = 0$ . The state of the circuit is given by the value of  $4Q_2 + 2Q_1 + Q_0$ .

[GATE : 2016]

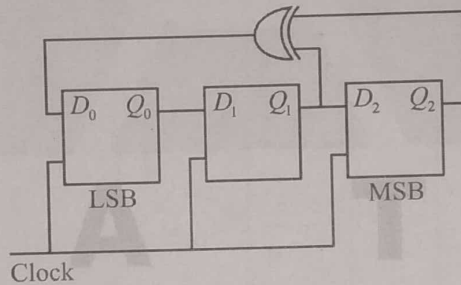


$Q_0$	$Q_1$	$Q_2$	$4Q_2 + 2Q_1 + Q_0$
1	0	0	1
0	1	0	2
1	0	1	5
1	1	0	3
1	1	1	7
0	1	1	6
0	0	1	4

Which one of the following is the correct state sequence of the circuit?

- (A) 1, 3, 4, 6, 7, 5, 2 (B) 1, 2, 5, 3, 7, 6, 4  
(C) 1, 2, 7, 3, 5, 6, 4 (D) 1, 6, 5, 7, 2, 3, 4

Q.103 Consider the partial implementation of a 2-bit counter using T flip-flops following the sequence 0-2-3-1-0, as shown below.

[GATE : 2004]

 

$$T_2 = Q_2 \oplus Q_1$$


$$T_1 = Q_2 \oplus Q_1$$

$$X = T_1$$

To complete the circuit, the input X should be

- (A)  $Q_2$  (B)  $Q_2 + Q_1$  (C)  $(Q_1 \oplus Q_2)'$  (D)  $(Q_1 \oplus Q_2)$

Q.104 Consider the following circuit.

 

[GATE : 2005]

$Q_0$	$Q_1$	$D_0$	$D_1$	$Q_0$	$Q_1$
0	0	0	1	1	1
1	1	0	1	0	1
0	1	1	0	1	0
1	0	0	0	0	0


$Q_0 \rightarrow Q_1$   $Q_0 \oplus Q_1$

The flip-flops are positive edge triggered D FFs. Each state is designated as a two bit string  $Q_0Q_1$ . Let the initial state be 00. The state transition sequence is:

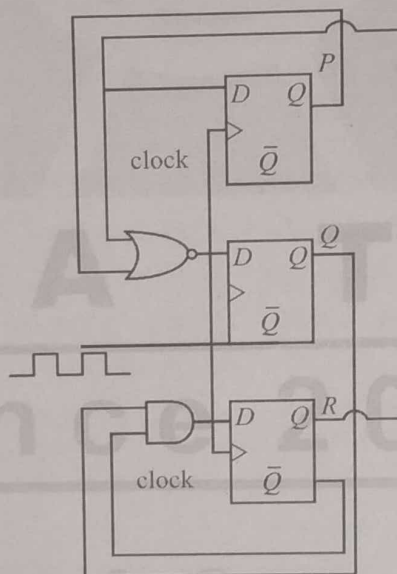- (A)  $00 \rightarrow 11 \rightarrow 01$  (B)  $00 \rightarrow 11$  (C)  $00 \rightarrow 10 \rightarrow 01 \rightarrow 11$  (D)  $00 \rightarrow 11 \rightarrow 01 \rightarrow 10$

Common Data for  
Questions 105 to 106

Consider the following circuit involving three D-type flip-flops used in a certain type of counter configuration. [GATE : 2011]



Q.105 If all the flip-flops were reset to 0 at power on, what is the total number of distinct outputs (states) represented by  $PQR$  generated by the counter? [GATE : 2011]

- (A) 3 (B) 4 (C) 5 (D) 6


Q.106 If at some instance prior to the occurrence of the clock edge,  $P$ ,  $Q$  and  $R$  have a value 0, 1 and 0 respectively, what shall be the value of  $PQR$  after the clock edge? [GATE : 2011]

- (A) 000 (B) 001 (C) 010 (D) 011

$$\begin{aligned} \bar{P} &= R \\ \bar{Q} &= P + R \\ \bar{R} &= Q + \bar{R} \end{aligned}$$



Q.107

 


The above synchronous sequential circuit built using JK flip-flops is initialized with  $Q_2Q_1Q_0 = 000$ . The state sequence for this circuit for the next 3 clock cycles is \_\_\_\_\_. [GATE : 2014]

- (A) 001, 010, 011 (B) 111, 110, 101 (C) 100, 110, 111 (D) 100, 011, 001

- Q.108** A positive edge-triggered D flip-flop is connected to a positive edge-triggered JK flip-flop as follows. The Q output of the D flip-flop is connected to both the J and K inputs of the JK flip-flop, while the Q output of the JK flip-flop is connected to the input of the D flip-flop. Initially, the output of the D flip-flop is set to logic one and the output of the JK flip-flop is cleared. Which one of the following is the bit sequence (including the initial state) generated at the Q output of the JK flip-flop when the flip-flops are connected to a free-running common clock? Assume that  $J = K = 1$  is the toggle mode and  $J = K = 0$  is the state-holding mode of the JK flip-flop. Both the flip-flops have non-zero propagation delays. [GATE : 2015]

- (A) 0110110..... (B) 0100100.... (C) 011101110... (D) 011001100...

 - Q.109** Consider a combination of T and D flip-flops connected as shown below. The output of the D flip-flop is connected to the input of the T flip-flop and the output of the T flip-flop is connected to the input of the D flip-flop. [GATE : 2017]



Initially, both  $Q_0$  and  $Q_1$  are set to 1 (before the 1<sup>st</sup> clock cycle). The outputs

- (A)  $Q_1Q_0$  after the 3<sup>rd</sup> cycle are 11 and after the 4<sup>th</sup> cycle are 00 respectively  
 (B)  $Q_1Q_0$  after the 3<sup>rd</sup> cycle are 11 and after the 4<sup>th</sup> cycle are 01 respectively  
 (C)  $Q_1Q_0$  after the 3<sup>rd</sup> cycle are 00 and after the 4<sup>th</sup> cycle are 11 respectively  
 (D)  $Q_1Q_0$  after the 3<sup>rd</sup> cycle are 01 and after the 4<sup>th</sup> cycle are 01 respectively

- Q.110** The next state table of a 2-bit saturating up-counter is given below. [GATE : 2017]

$Q_1$	$Q_0$	$Q_1^+$	$Q_0^+$	$T_1$	$T_2$
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	0
1	1	1	1	0	0

The counter is built as a synchronous sequential circuit using T flip-flops. The expression for  $T_1$  and  $T_0$  are

(A)  $T_1 = Q_1Q_0, T_0 = \overline{Q_1}Q_0$

(C)  $T_1 = Q_1 + Q_0, T_0 = \overline{Q_1} + \overline{Q_0}$

(B)  $T_1 = \overline{Q_1}Q_0, T_0 = \overline{Q_1} + \overline{Q_0}$

(D)  $T_1 = \overline{Q_1}Q_0, T_0 = Q_1 + Q_0$

